 


Digital System Clocking:

High-Performance and Low-Power Aspects


Vojin G. Oklobdzija, Vladimir M. Stojanovic, Dejan M. Markovic, Nikola M. Nedovic

Chapter 2: Clocked Storage Elements Operation



Wiley-Interscience and IEEE Press, January 2003

Evolution of a Latch :

 


(a) keeper; information is latched


(b) S-R latch; information can be modified

(c) S-o-P latch; S-R latch that can implement a function - IMPORTANT!

Adding Clock Control to a Latch

 

*D*_(a)

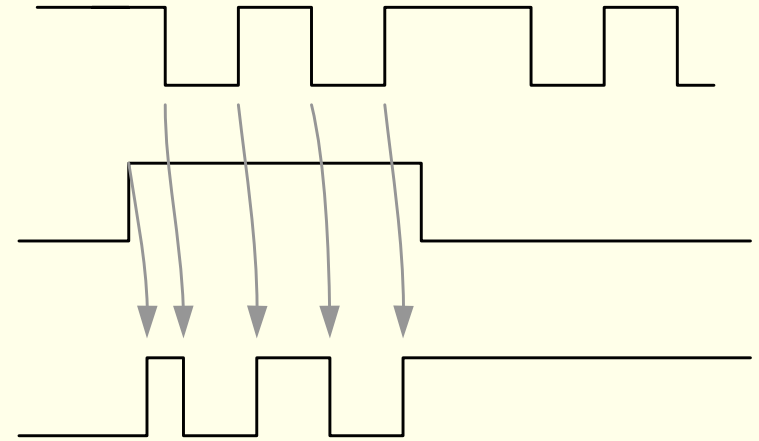


(b)


Latching can be done only when clock is active, otherwise no change is allowed:

(a) Clocked D-latch; (b) timing diagram of clocked D-latch

Importance of Latch S-o-P Configuration

 


(a)

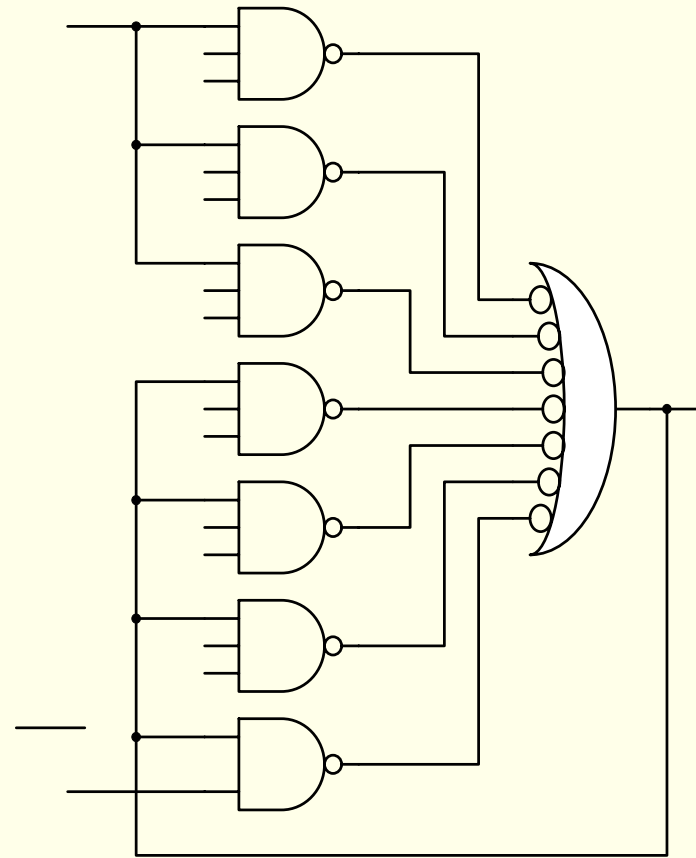

(b)


(a) Basic Earl's Latch; (b) Implementing the Carry function

Master-Slave Latch

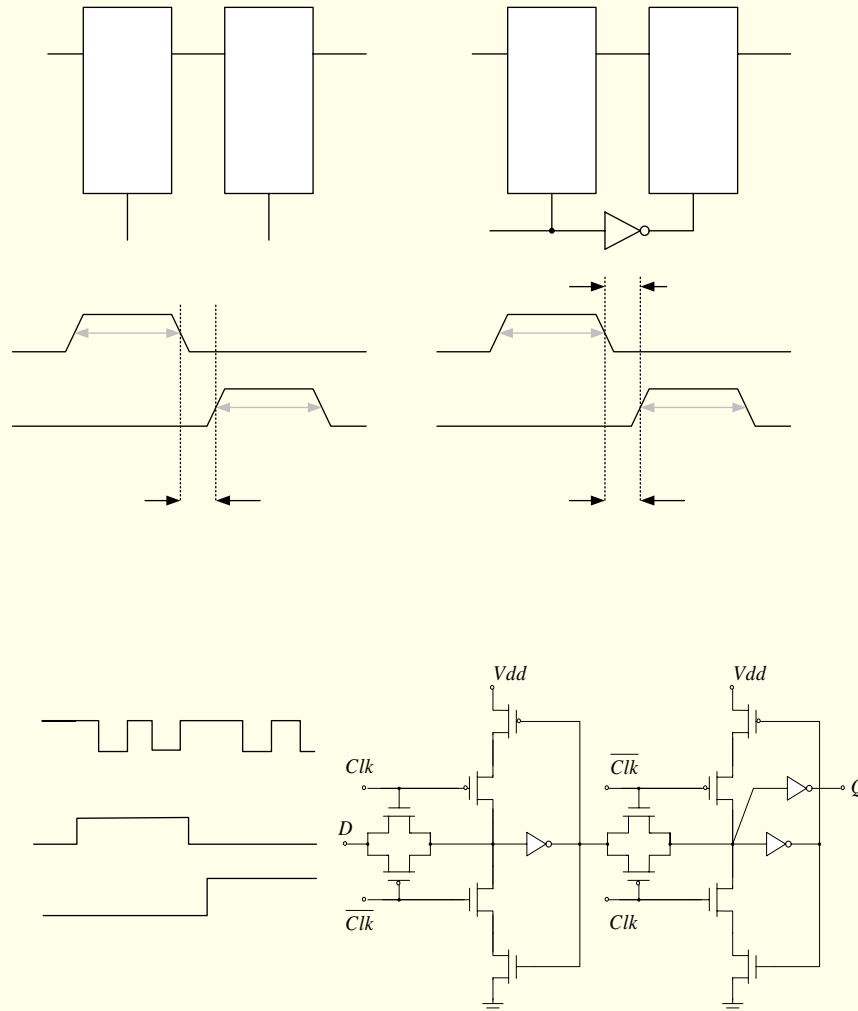

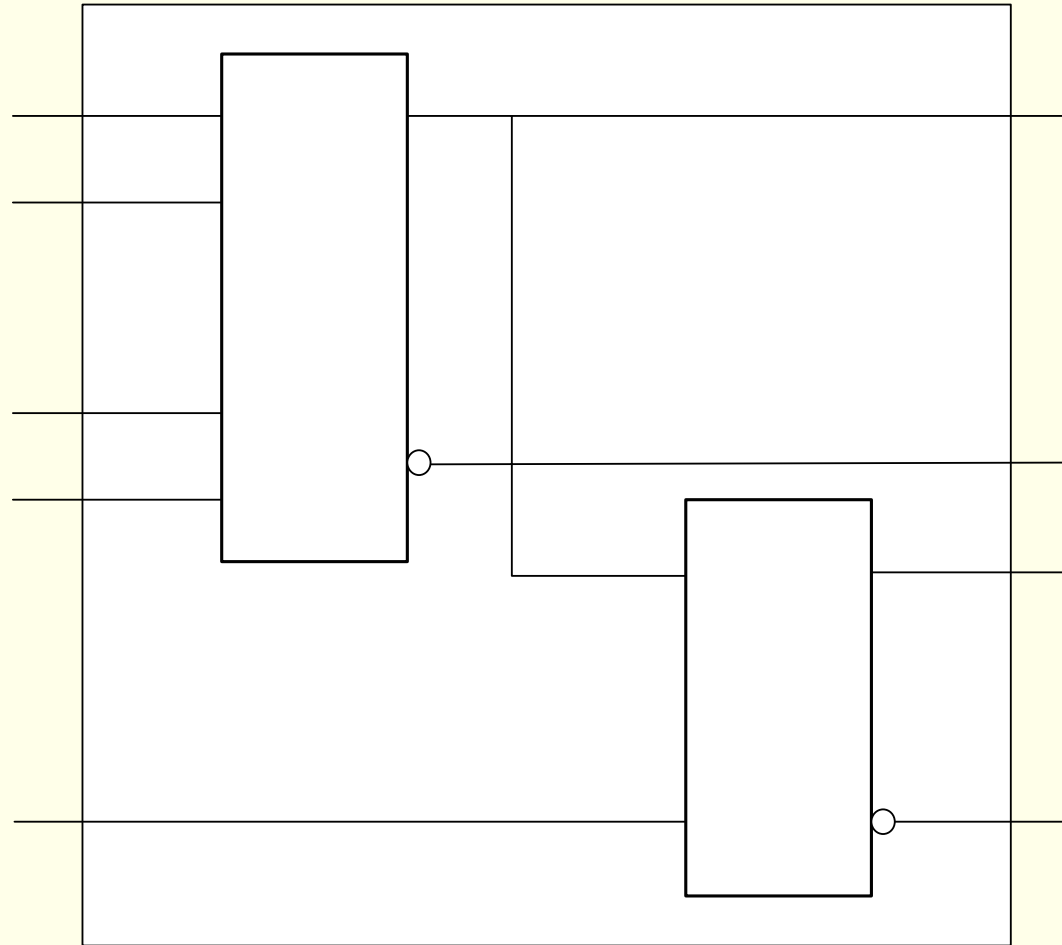(a) non-overlapping clocks; (b) single external clock; (c) timing diagram;
 (d) PowerPC 603 MS Latch (Gerosa, JSSC 12/94), Copyright © 1994 IEEE


IBM LSSD Compatible Clocked Storage Element




System Data D

True-single-phase-clock (TSPC) M-S latch

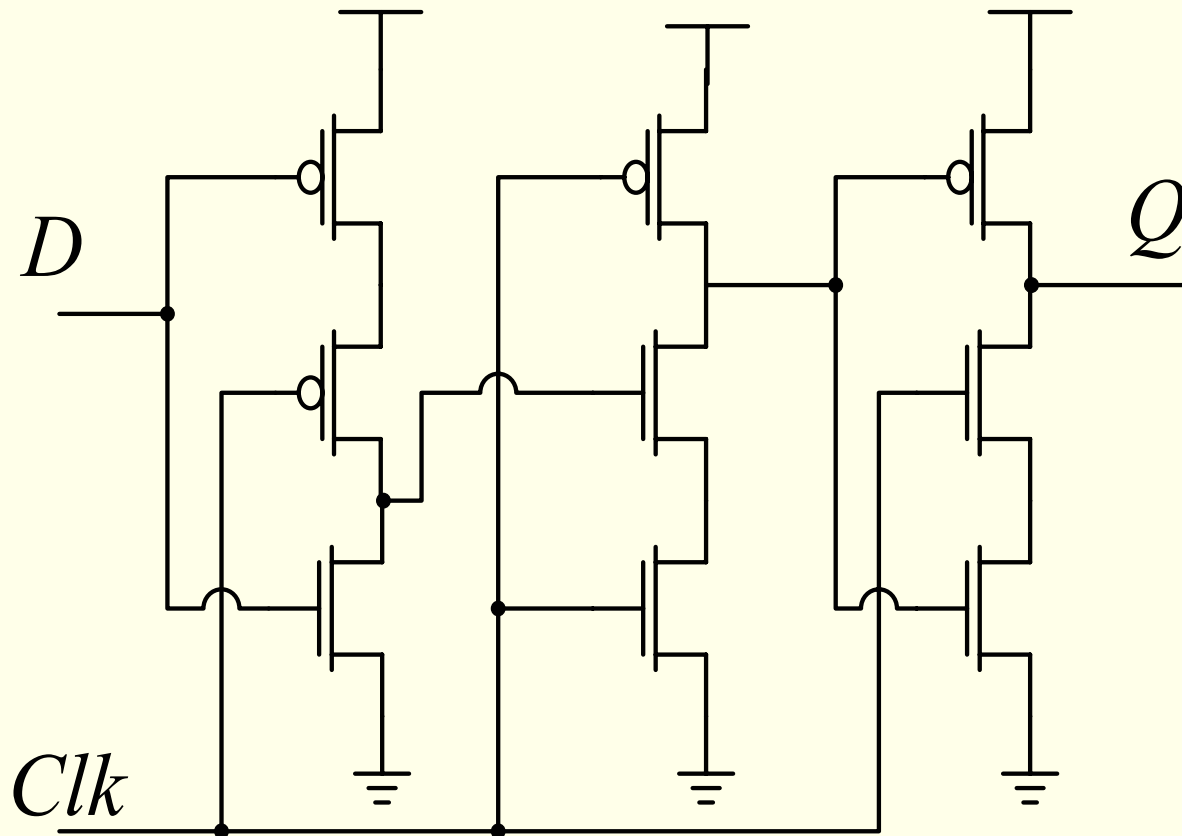Yuan and Svenson (1989), Copyright © 1989 IEEE





TSPC M-S Latch Operation

 

Pulse latch

(Kozu et al. 1996) Copyright © 1996 IEEE

  


(a) local clock generator; (b) single latch; (c) clock signals


Clk_{in}

Pulse latch: Intel's explicit pulsed latch

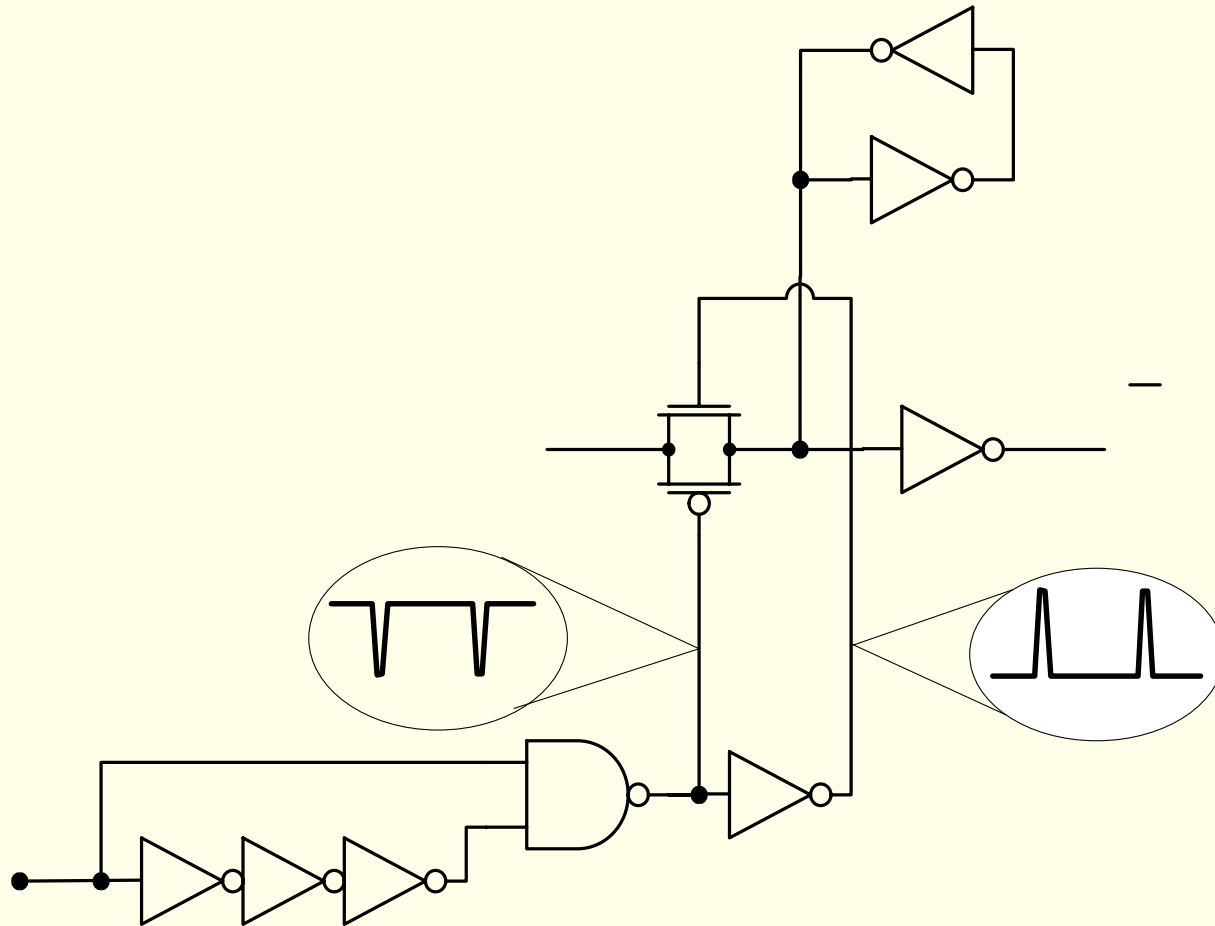
(Tschanz et al. 2001), Copyright © 2001 IEEE



Flip-flop

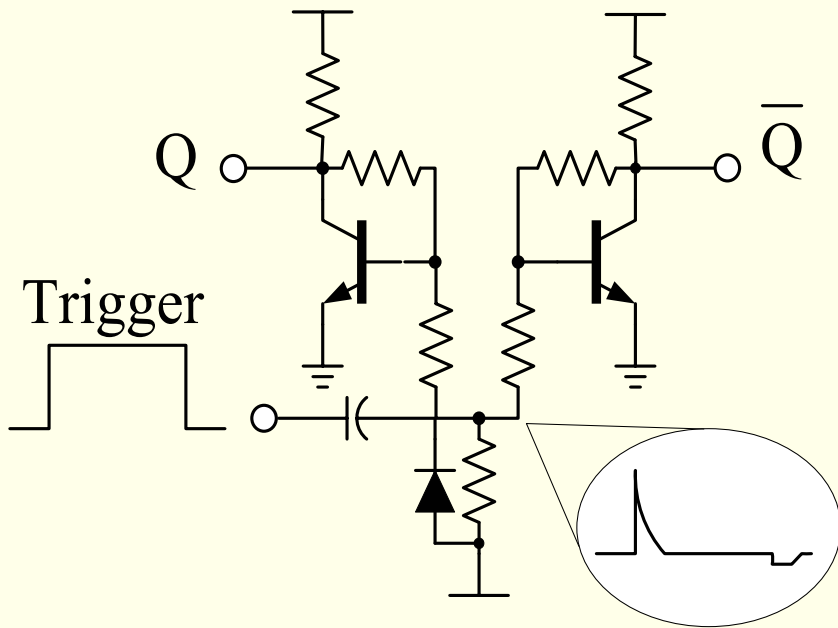


(a)

 

V_{DD} (b)


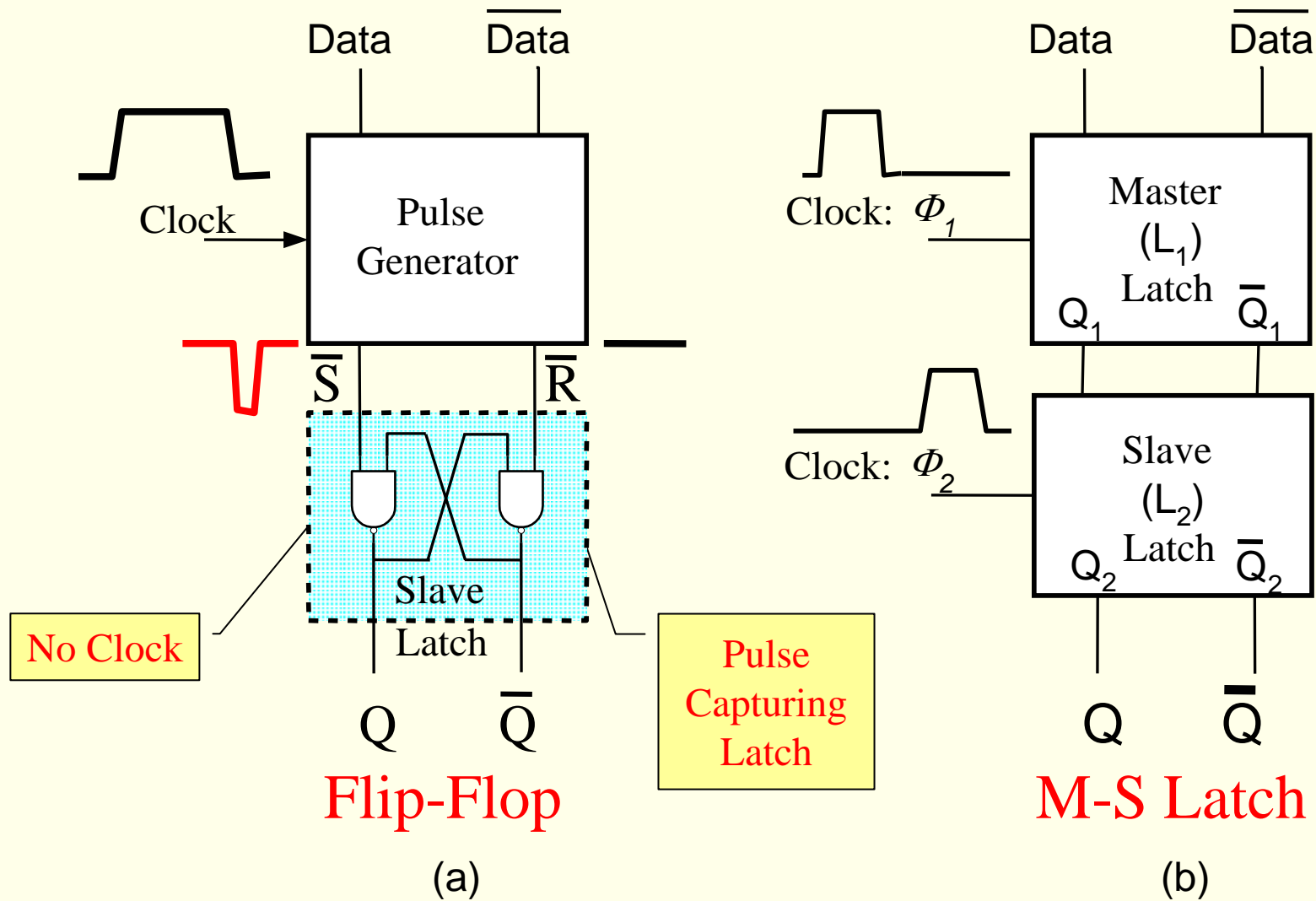
(a) Early version of a flip-flop; (b) PDP-8 direct set-reset sequential element

Difference between Flip-flop and M-S Latch



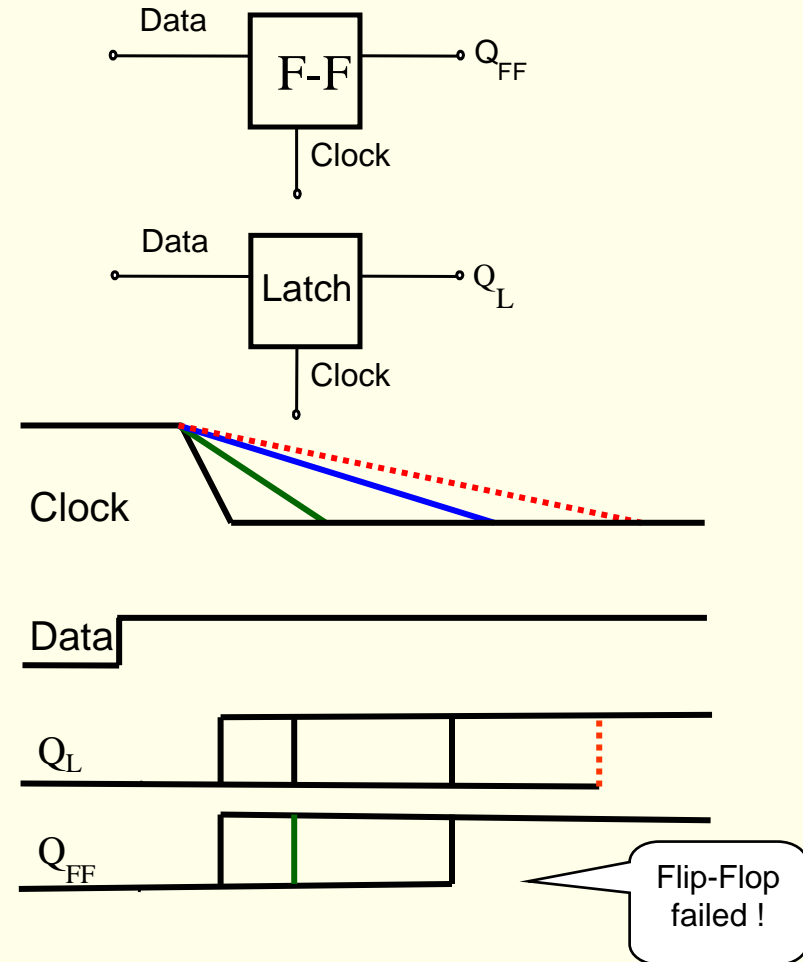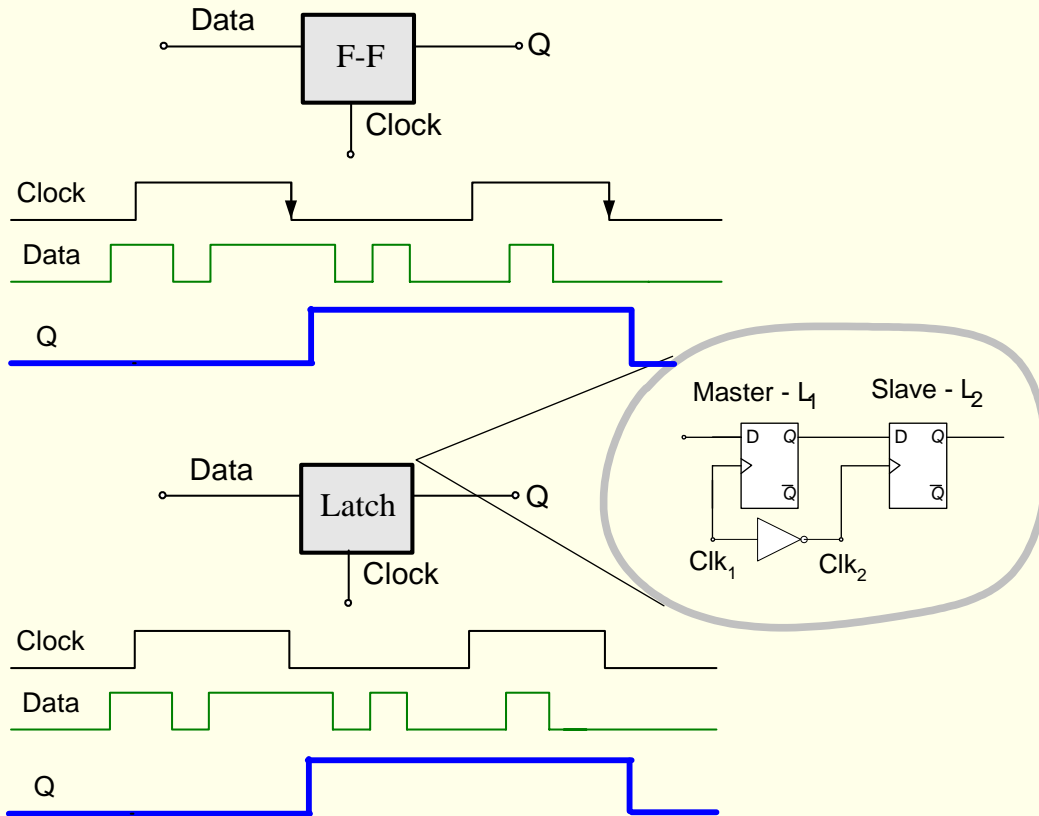
(a) General flip-flop structure; (b) general M-S latch structure

Black-box view of the Flip-flop and M-S latch





Experiment causing the flip-flop to fail while the M-S latch is still operational

Texas Instruments SN7474 Flip-flop

 


Very much used and analyzed

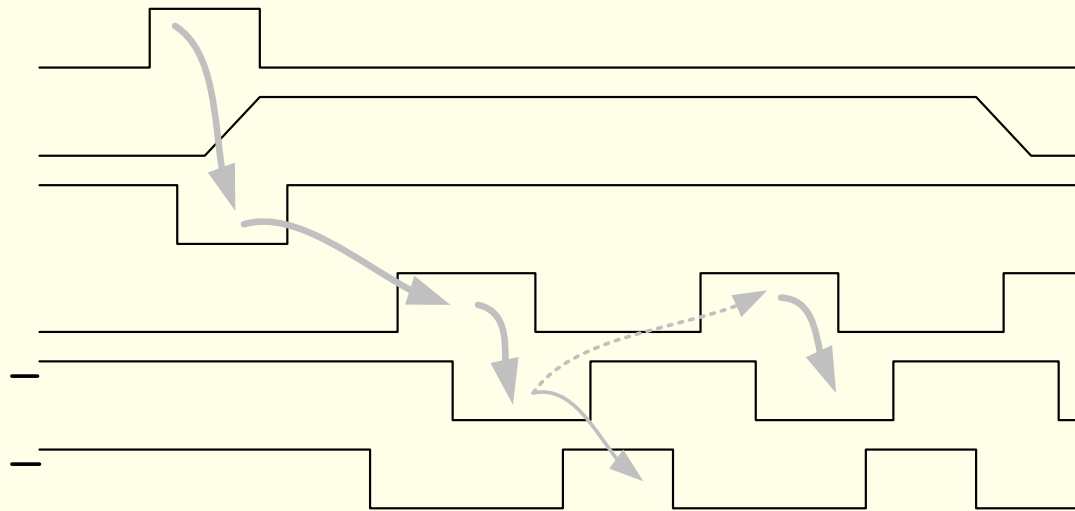 Pulse generator block of SN7474: malfunctioning due to a gate-delay




D

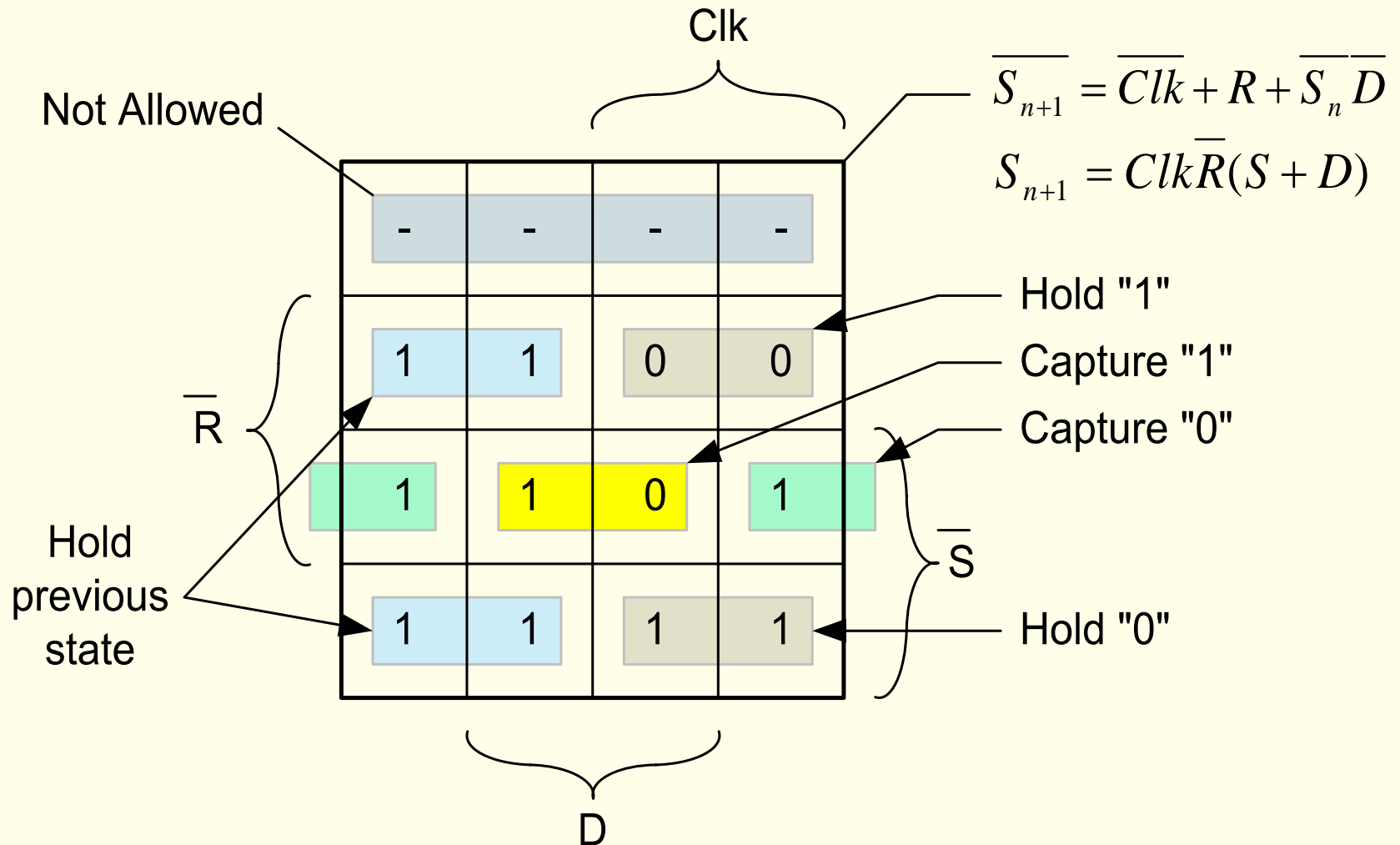
Systematic Derivation of a FF using Karnaugh map



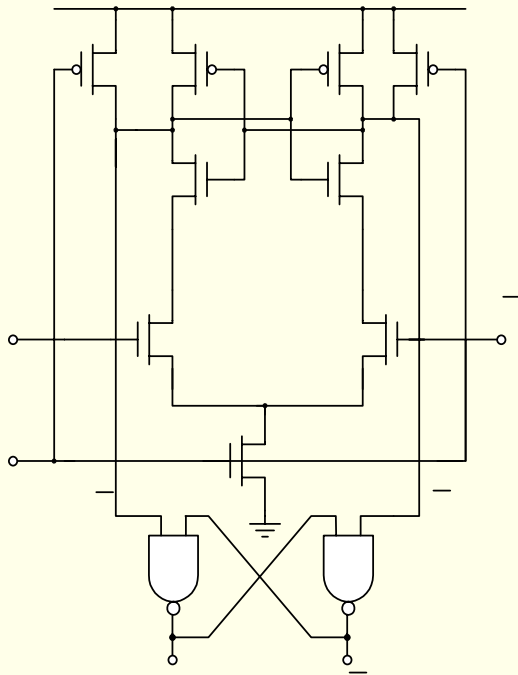
Derivation of the pulse-generating stage of a flip-flop (only the S_n signal is shown)



(a)

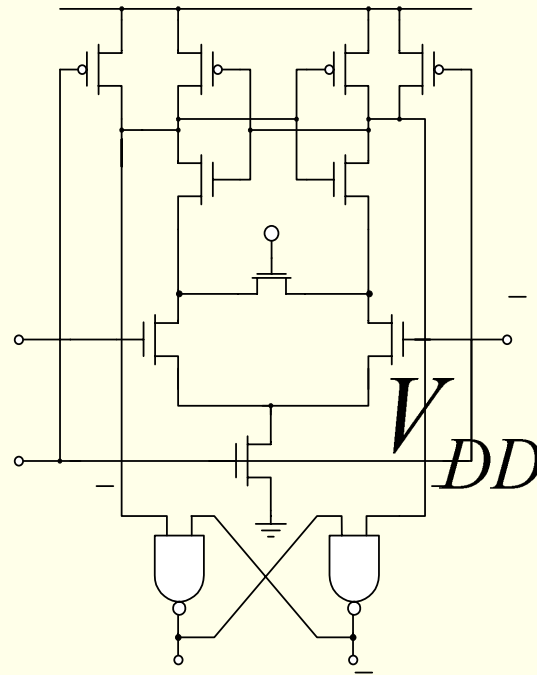


(b)

 


(c)

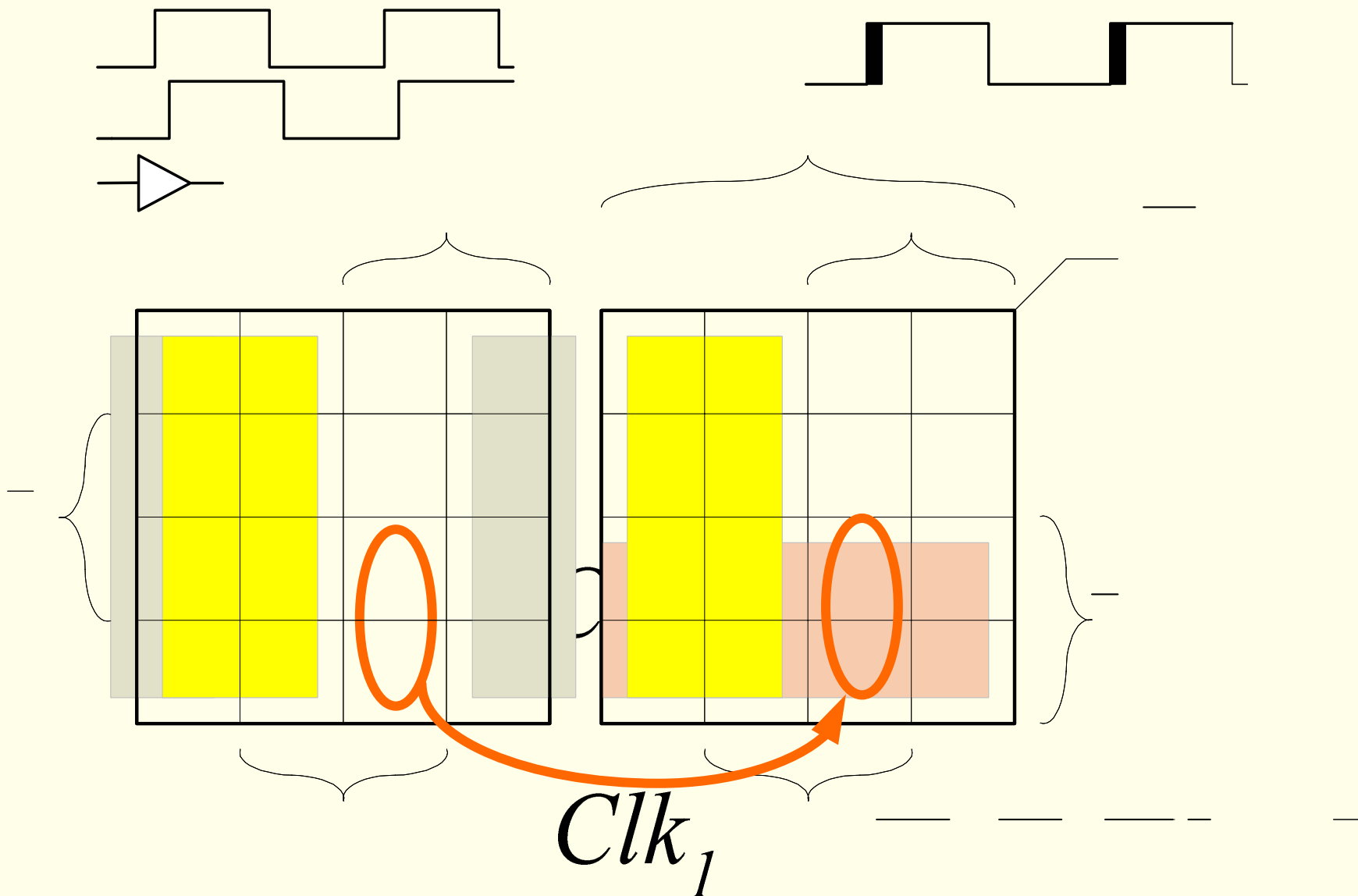- (a) Pulse generator stage of the sense-amplifier flip-flop. (Madden and Bowhill, 1990);
 (b) Improvement for floating nodes. (Dobberpuhl, 1997);
 (c) Pulse generator stage improvement by proper design. (Nikolic and Oklobdzija, 1999).


Creating the time reference points for opening and shutting the flip-flop



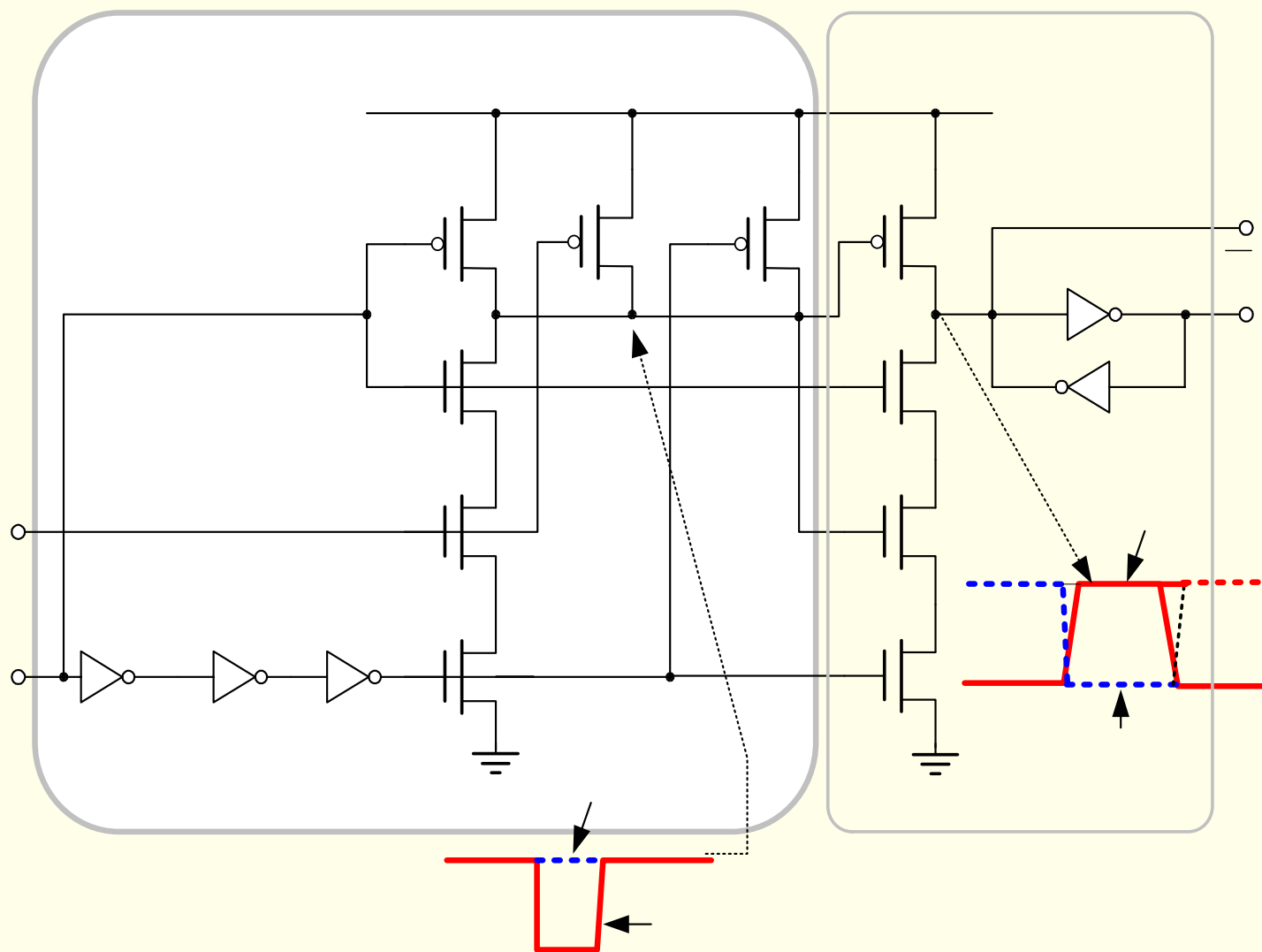Hybrid-Latch Flip-Flop (HLFF) introduced by Partovi et al.




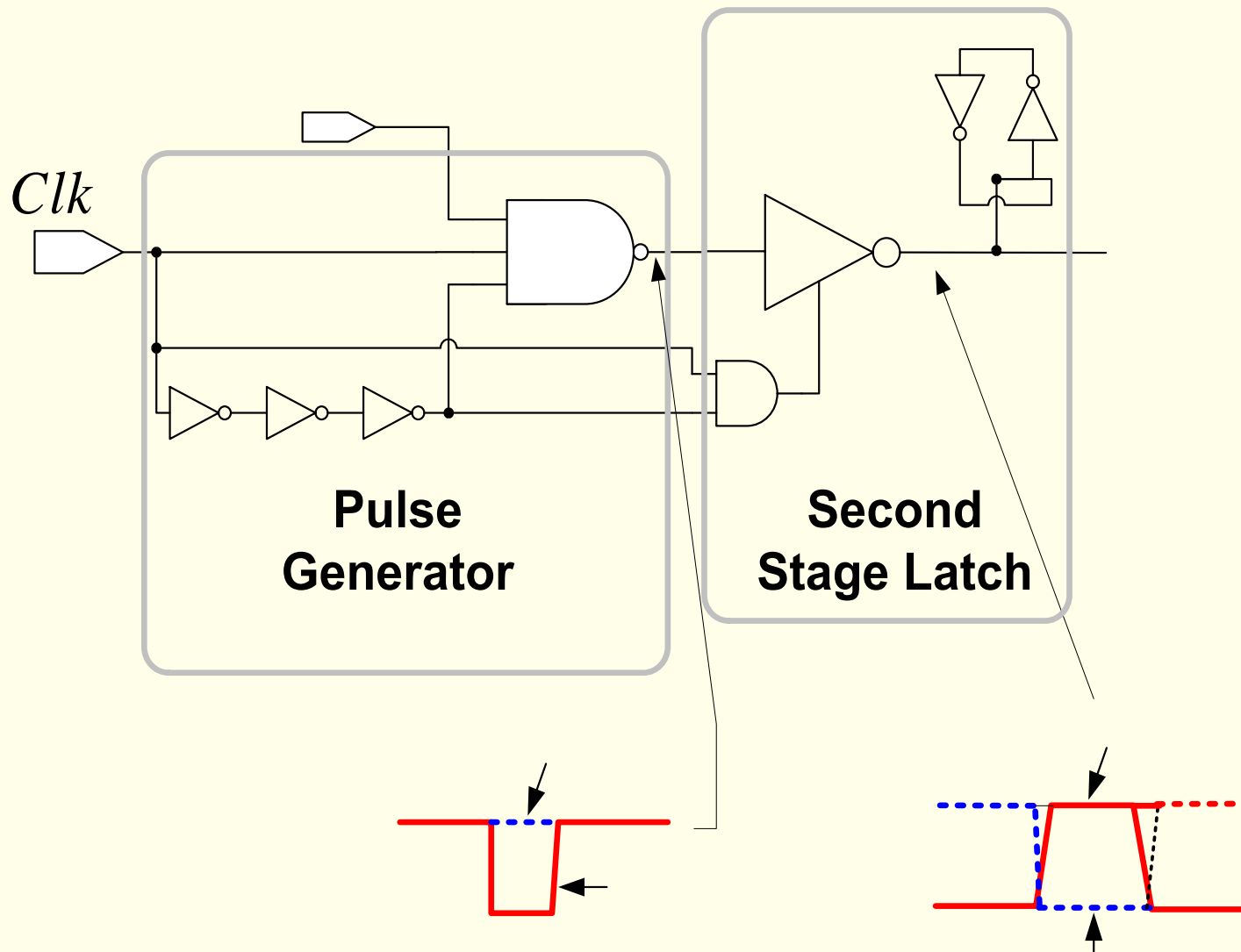Logic representation of Partovi's flip-flop (HLFF)




Systematically derived single-ended flip-flop

(according to the slide no. 18)

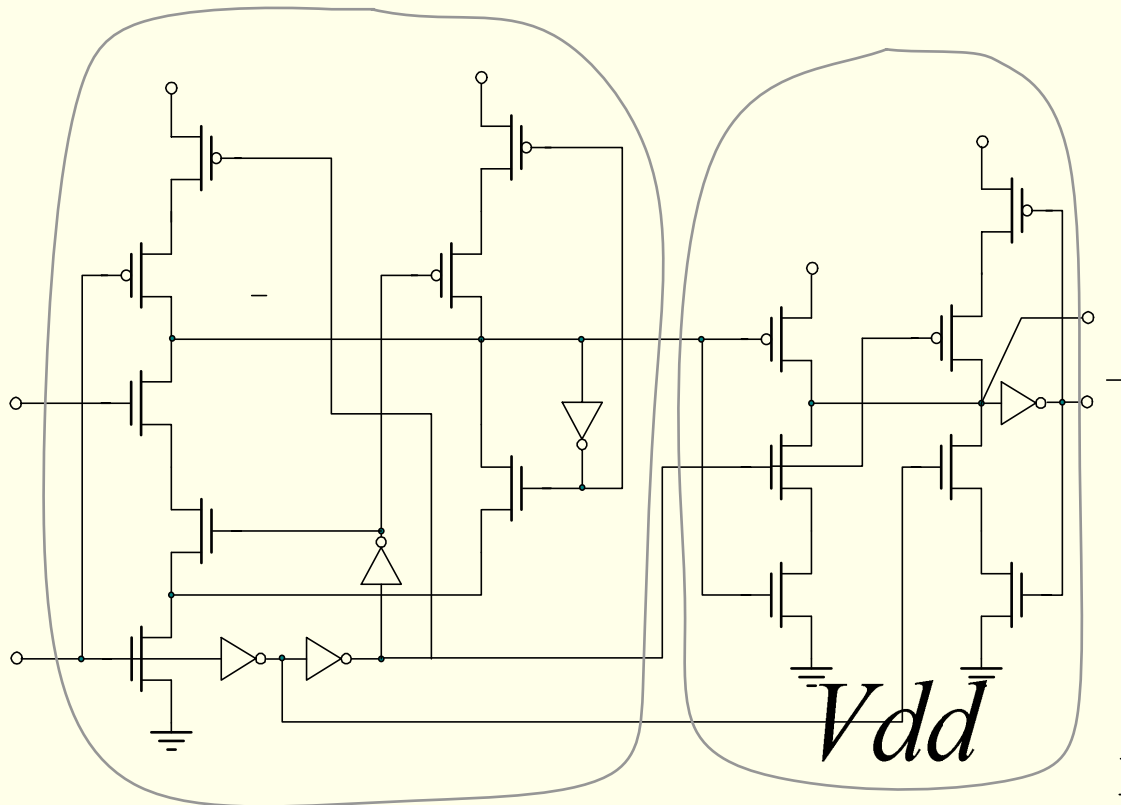

(a)

 

(b)

(a) circuit diagram;

(b) logic representation.

(Nedovic and Oklobdzija, 2000). Copyright © 2000 IEEE

M_{P1}

M_{P3}