 


Digital System Clocking:

High-Performance and Low-Power Aspects

Vojin G. Oklobdzija, Vladimir M. Stojanovic, Dejan M. Markovic, Nikola M. Nedovic

Chapter 6: Low-Energy System Issues



Wiley-Interscience and IEEE Press, January 2003

Clocking Energy

- System Issues
 - Increasing clock frequency
 - Low skew requirements
 - Deeper pipelining
- Increased Clocking Energy
 - Focus on energy minimization
- Methods for Energy Reduction
 - Supply voltage scaling
 - Alternate circuit topology
 - New clocking strategies

Switching Energy

Clock is the highest activity signal \Rightarrow Switching energy is dominant

$$E_{\text{switching}} = \sum_{i=1}^N \alpha_{0-1}(i) \cdot C_i \cdot V_{\text{swing}}(i) \cdot V_{DD}$$


*α - probability of a 0-1 transition
 C_i - total switched capacitance at node i
 $V_{\text{swing}}(i)$ - voltage swing at node i
 V_{DD} - supply voltage
 N - number of nodes*

*Energy is best reduced by scaling down V_{DD} ,
but this also means performance degradation*

Supply Voltage Scaling

- Supply voltage is the most dominant tuning knob for energy reduction
 - Not always possible due to performance requirements
- Flip-flop speed scales favorably with V_{DD} compared to standard CMOS inverter
 - Improved slow-path requirements
- Internal race immunity tracks scaling of an inverter
 - Same fast-path requirements

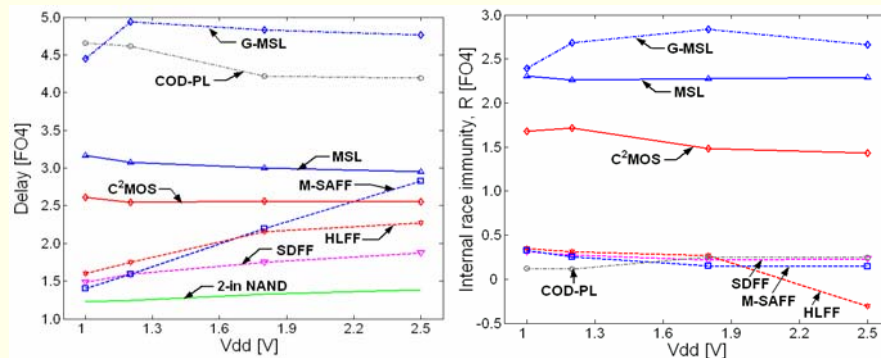Pulsed Designs Scale the Best with V_{DD}



(a)

(b)

(Delay is normalized to FO4 at its respective V_{DD} . FO4 as defined in this example increases with $V_{DD} \Rightarrow$ performance degradation)

*Impact of Vdd on (a) delay, and (b) internal race immunity (0.25 μm , light load).
(Markovic et al. 2001), Copyright © 2001 IEEE*

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

5

Minimizing Switched Capacitance

- Clocked capacitances are the most important to minimize due to their high switching activity
- Reduce C_{sw} by circuit sizing that takes into account both energy and performance
 - Topology dependent
 - Lower limit imposed by the noise requirements

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

6

Other Energy Reduction Techniques

- Low-Swing Circuit Techniques
 - Reduced-swing Clk drivers
 - CSE redesign
 - N-only CSEs with Low-Vcc Clk
- Clock Gating
 - Global
 - Local
- Dual-Edge Triggering
 - Latch-mux
 - Pulsed-latch
 - Flip-flop

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

7

Other Energy Reduction Techniques


- Low-Swing Circuit Techniques
 - Reduced-swing Clk drivers
 - CSE redesign
 - N-only CSEs with Low-Vcc Clk
- Clock Gating
 - Global
 - Local
- Dual-Edge Triggering
 - Latch-mux
 - Pulsed-latch
 - Flip-flop

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

8

 Low-Swing Clocking, Option #1: Clock Driver Re-design



50% power reduction with half-swing clock
(minus some penalty in clock drivers)

Clock driver for half-swing clocking
(Kojima et al. 1995), Copyright © 1995 IEEE


Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

9

Low-Swing Clocking, Option #2: CSE Re-design

PMOS does not
fully turn-off

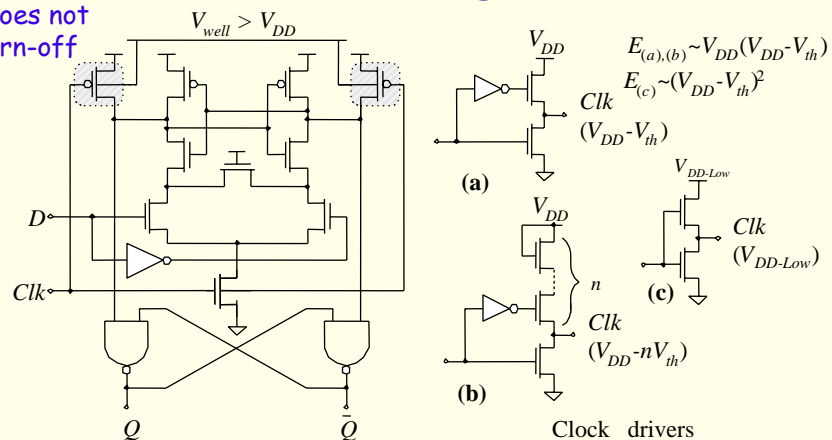


Reduced clock-swing flip-flop
(Kawaguchi and Sakurai, 1998), Copyright © 1998 IEEE

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

10

 Low-Swing Clocking, Option #3: N-only CSEs




N-only clocked transistors, M-S Latch Example
(N_1 and N_2 improve pull-up on S_M)

N-Only clocked M-S latch

Other Energy Reduction Techniques

- Low-Swing Circuit Techniques
 - Reduced-swing Clk drivers
 - CSE redesign
 - N-only CSEs with Low-Vcc Clk
- Clock Gating
 - Global
 - Local
- Dual-Edge Triggering
 - Latch-mux
 - Pulsed-latch
 - Flip-flop

 
Clock Gating, Option #1: Global Clock Gating



Used to save clocking energy when data activity is low

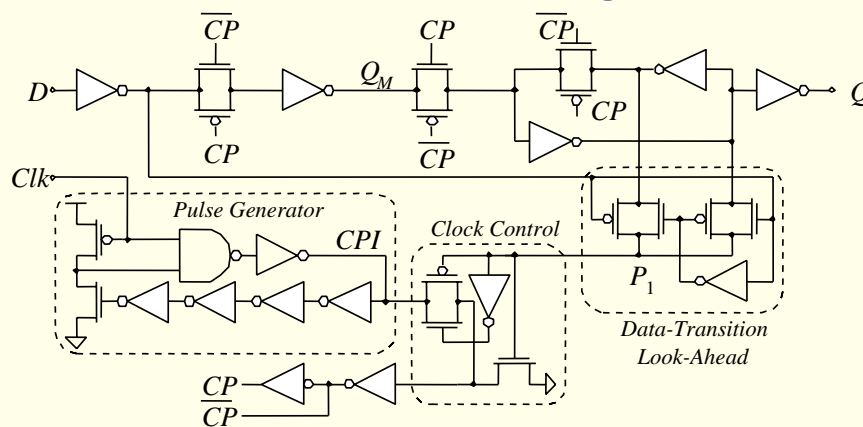*(a) Nongated clock circuit, (b) gated clock circuit.
(Kitahara et al. 1998), Copyright © 1998 IEEE*


Clock Gating, Option #2: Local Clock Gating



*Data-transition look-ahead latch
(Nogawa and Ohtomo, 1998), Copyright © 1998 IEEE*

Local Clock Gating, Another Example

Clk enabled only when $D \neq Q$

 

*Conditional capture flip-flop
(Kong et al. 2000), Copyright © 2000 IEEE*

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

15

Other Energy Reduction Techniques


- Low-Swing Circuit Techniques
 - Reduced-swing Clk drivers
 - CSE redesign
 - N-only CSEs with Low-Vcc Clk
- Clock Gating
 - Global
 - Local
- Dual-Edge Triggering
 - Latch-mux
 - Pulsed-latch
 - Flip-flop

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

16

 Dual-Edge Triggering, Option #1: Latch-Mux



Used to save clocking energy regardless of data activity!


Dual-edge-triggered latch-mux design

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

17

DET Latch-Mux: Circuit Example

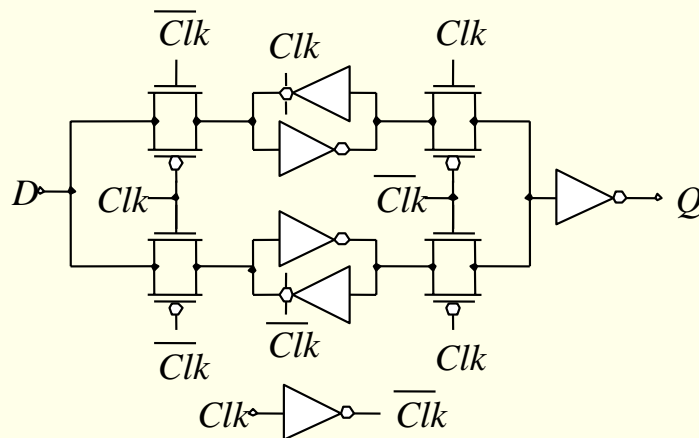


*Dual-edge-triggered latch-mux circuit
(Llopis and Sachdev, 1996), Copyright © 1996 IEEE*

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic


18

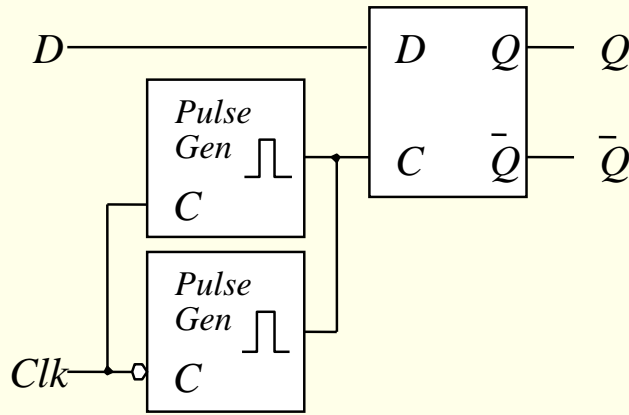Dual-Edge Triggering, Option #2: Pulsed-Latch




Dual-edge-triggered pulsed-latch design

DET Pulsed-Latch: Circuit Examples

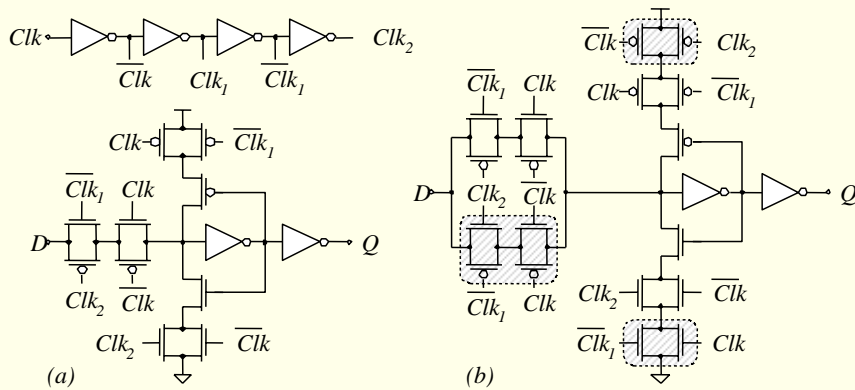

Pulsed-latch: (a) single-edge-triggered; (b) dual-edge-triggered

Dual-Edge Triggered Flip-Flop

 


Dual-edge-triggered flip-flop design

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

21

DET Flip-Flop: Circuit Example

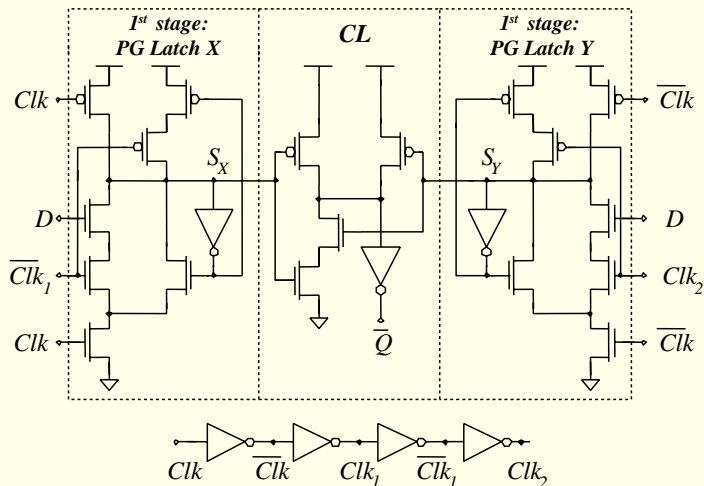


DET symmetric pulse-generator flip-flop

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic


22

Clock Distribution for DET CSEs

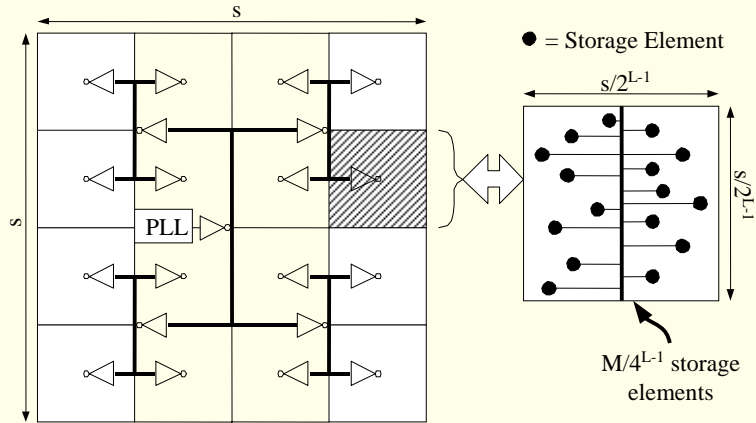

H-tree clock distribution network

Clocking Power: SET vs. DET

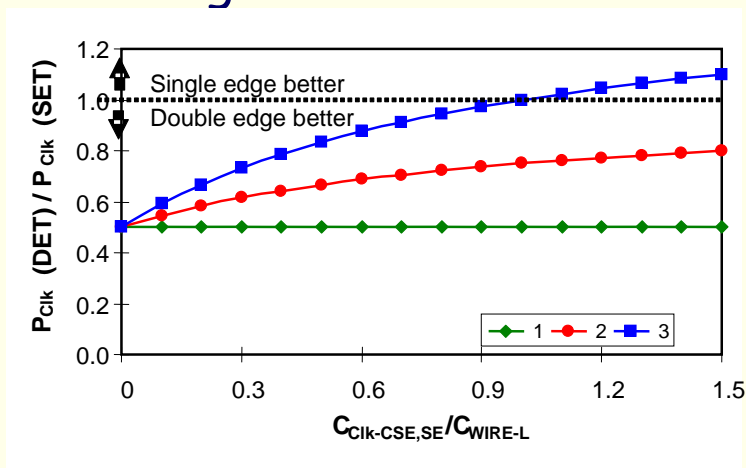


DET wins if the total clock load capacitance is below 2x the capacitance of a SET design

Glitch Tolerant Design


- Are CSEs that are the best in terms of active power also favorable in terms of glitch power?
- The opposite is true
- So, let's investigate how glitch power scales with data and glitching activity

Average Glitching Energy in CSEs

 

Comparison of average glitching energy in CSEs (Markovic et al. 2001), Copyright © 2001 IEEE

 Comparison of $E_{\text{glitching}}$ and $E_{\text{switching}}$



Glitching energy as a percentage of switching energy in representative CSEs showing the greatest glitch sensitivity of the gated designs

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

27

Summary

- Energy best reduced by V_{DD} scaling
 - Penalty in performance
- Reducing Clk swing only reduces E_{clk}
 - Still penalty in performance
- Clock gating
 - Reduces E_{clk} at low-activity
 - No penalty in perf. if gating is outside crit-path
- Dual-Edge Triggering
 - Reduces E_{clk} ideally by 2x
 - Small or no performance degradation

Nov. 14, 2003

Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic

28