 


# Digital System Clocking:

## High-Performance and Low-Power Aspects

Vojin G. Oklobdzija, Vladimir M. Stojanovic, Dejan M. Markovic, Nikola M. Nedovic

### Chapter 9: Microprocessor Examples



Wiley-Interscience and IEEE Press, January 2003

## Microprocessor Examples

- Clocking for Intel® Microprocessors
  - IA-32 Pentium® Pro
  - First IA-64 Microprocessor
  - Pentium 4
- Sun Microsystems UltraSPARC-III® Clocking
  - Clocking and CSEs
- Alpha® Clocking: A Historical Overview
  - Clocking and CSEs
- IBM® Microprocessors
  - Level-Sensitive Scan Design
  - Examples of CSEs

## Microprocessor Examples


- Clocking for Intel® Microprocessors
  - IA-32 Pentium® Pro
  - First IA-64 Microprocessor
  - Pentium 4
- Sun Microsystems UltraSPARC-III® Clocking
  - Clocking and CSEs
- Alpha® Clocking: A Historical Overview
  - Clocking and CSEs
- IBM® Microprocessors
  - Level-Sensitive Scan Design
  - Examples of CSEs

## Intel® Microprocessor Features

|                        | Pentium® II        | Pentium® III       | Pentium® 4         |
|------------------------|--------------------|--------------------|--------------------|
| <b>MPR Issue</b>       | June 1997          | April 2000         | Dec 2001           |
| <b>Clock Speed</b>     | 266 MHz            | 1GHz               | 2GHz               |
| <b>Pipeline Stages</b> | 12/14              | 12/14              | 22/24              |
| <b>Transistors</b>     | 7.5M               | 24M                | 42M                |
| <b>Cache (I/D/L2)</b>  | 16k/16K/-          | 16K/16K/256K       | 12K/8K/256K        |
| <b>Die Size</b>        | 203mm <sup>2</sup> | 106mm <sup>2</sup> | 217mm <sup>2</sup> |
| <b>IC Process</b>      | 0.28µm, 4M         | 0.18µm, 6M         | 0.18µm, 6M         |
| <b>Max Power</b>       | 27W                | 23W                | 67W                |

*Source: Microprocessor Report Journal*

## IA-32 Pentium® Pro

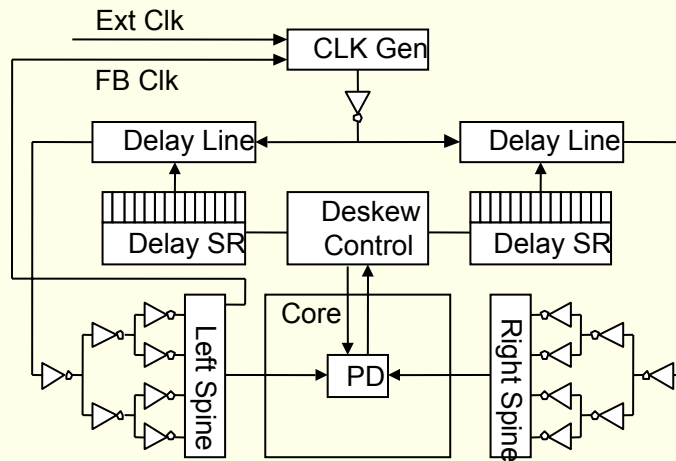


*Clock distribution network with deskewing circuit  
(Geannopoulos and Dai 1998), Copyright © 1998 IEEE*

## Adaptive Deskewing Technique


- Equalization of two clock distribution spines by compensating for delay mismatch
  - Delay lines
  - Phase detector
  - Controller
- Result: global clock skew of only 15ps
  - 0.25 $\mu$ m technology
  - 7.5M transistors

# IA-32 Pentium® Pro

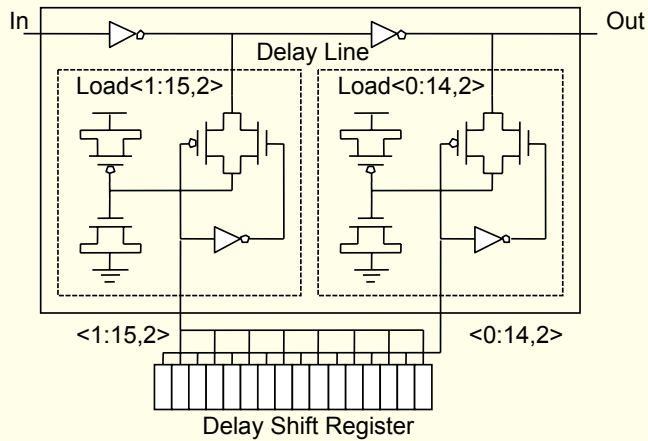


*Delay shift register  
(Geannopoulos and Dai 1998), Copyright © 1998 IEEE*

# IA-32 Pentium® Pro

 

*Phase detector  
(Geannopoulos and Dai 1998), Copyright © 1998 IEEE*

## First IA-64 Microprocessor

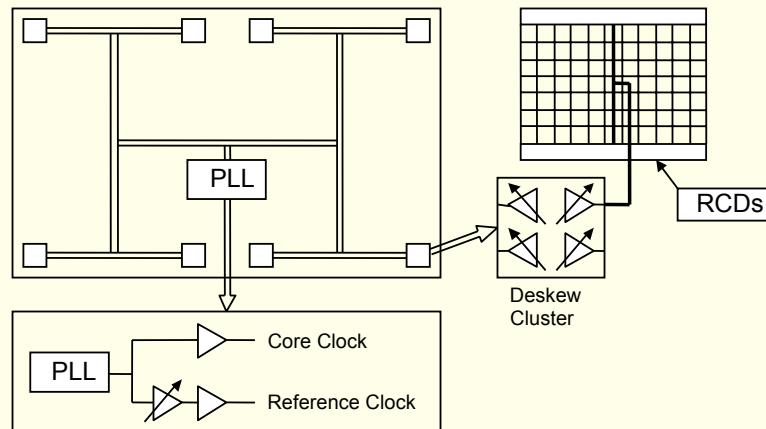


*Clock distribution topology  
(Rusu and Tam 2000), Copyright © 2000 IEEE*

## Programmable Deskew Units


- Strategy similar to that in IA-32
- External differential clock
  - System bus frequency
- PLL generates internal clock
  - 2x frequency
- Clock distribution architecture
  - Balanced global clock tree
  - Multiple deskew buffers
  - Multiple local clock buffers

# First IA-64 Microprocessor

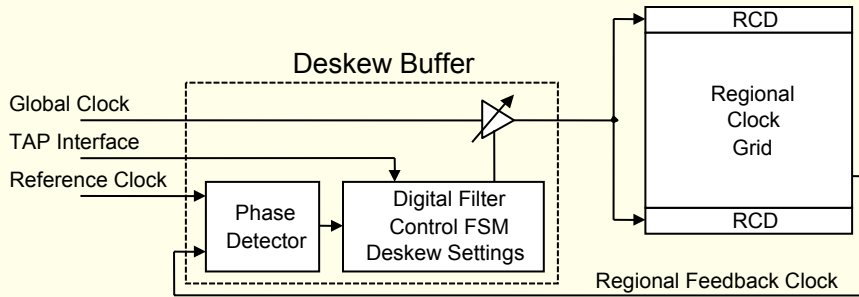


*Deskew buffer architecture  
(Rusu and Tam 2000), Copyright © 2000 IEEE*

# First IA-64 Microprocessor

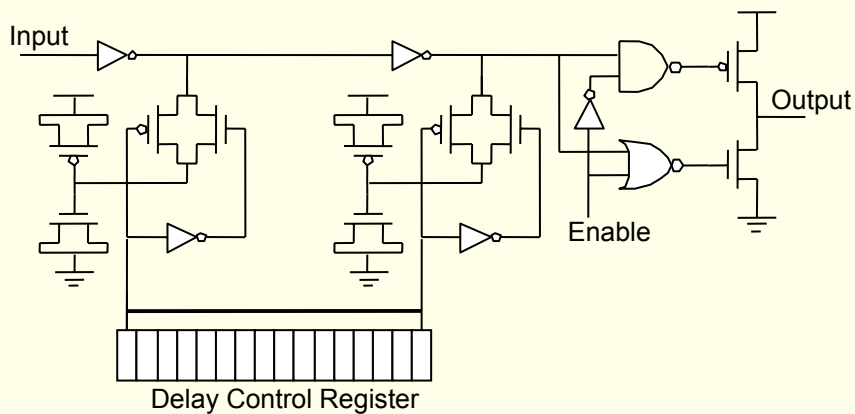


*Digitally controlled delay line  
(Rusu and Tam 2000), Copyright © 2000 IEEE*

# First IA-64 Microprocessor

 


*Simulated regional clock-grid skew  
(Rusu and Tam 2000), Copyright © 2000 IEEE*

# First IA-64 Microprocessor

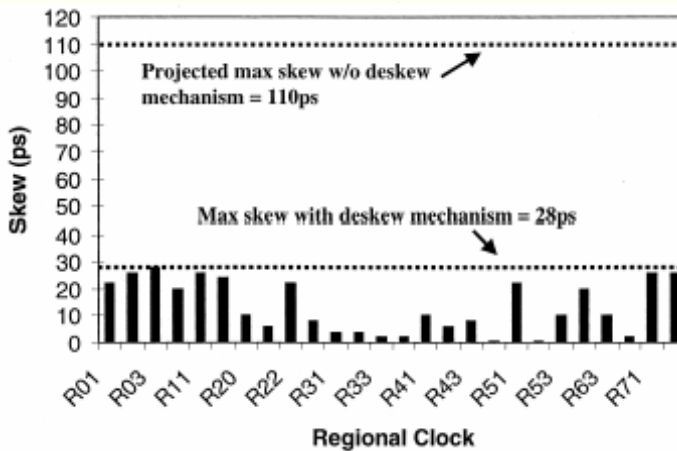

*Measured regional clock skew  
(Rusu and Tam 2000), Copyright © 2000 IEEE*

# Pentium® 4

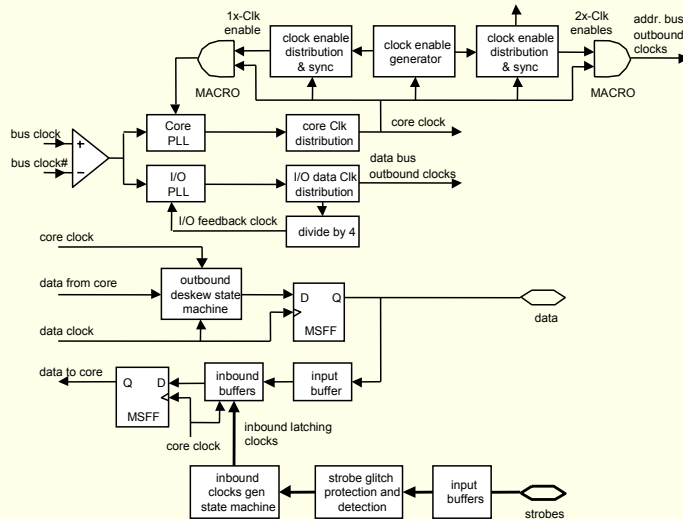


*Core and I/O clock generation  
(Kurd et al. 2001), Copyright © 2001 IEEE*

## Multi-GHz Clock Network in Pentium 4

- Three core and three I/O frequencies (total 6 frequencies running concurrently)
- Differential off-chip reference clock
  - PLL synthesizes core and I/O clocks
- Global core clock distribution
  - 47 independent clock domains
  - Each domain has 5-bit deskew control register
- Clock skew < 20ps




# Pentium® 4

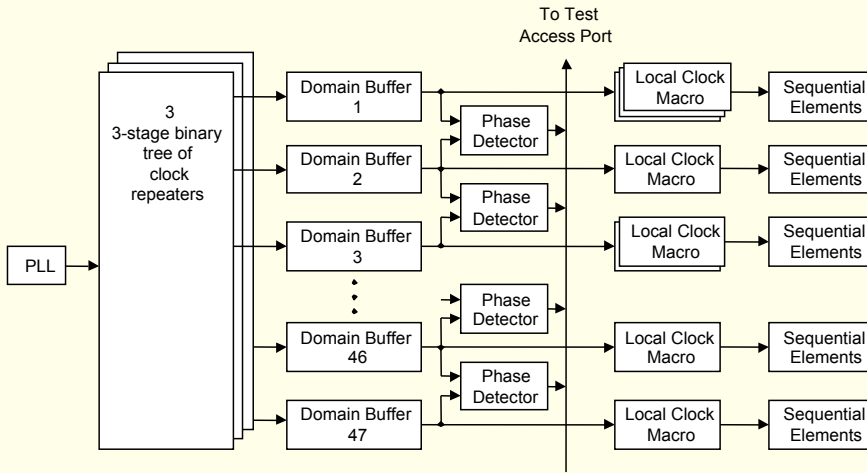

Logical diagram of core clock distribution (Kurd et al. 2001), Copyright © 2001 IEEE

# Pentium® 4

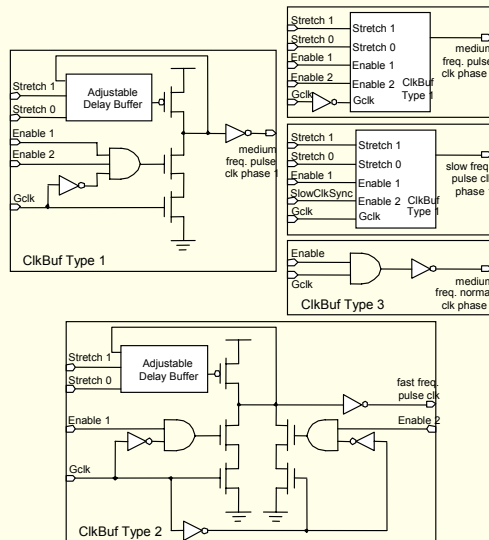

Example of local clock buffers generating various frequency, phase and types of clocks (Kurd et al. 2001), Copyright © 2001 IEEE

## Intel Clocking: Summary

- Increasing clock speeds and die size
  - Balancing the clock skew in large designs using simple RC trees is becoming less effective
- Insertion delay 7-8FO4 due to increased die
  - Comparable to the clock period
- Clock skew control has been getting harder to due to increased PVT variations
- Inductive effects at multi-GHz rates
- Use of active deskewing circuits

## Microprocessor Examples

- Clocking for Intel® Microprocessors
  - IA-32 Pentium® Pro
  - First IA-64 Microprocessor
  - Pentium 4
- Sun Microsystems UltraSPARC-III® Clocking
  - Clocking and CSEs
- Alpha® Clocking: A Historical Overview
  - Clocking and CSEs
- IBM® Microprocessors
  - Level-Sensitive Scan Design
  - Examples of CSEs


## UltraSPARC® Family Characteristics

|                          | UltraSPARC-I®            | UltraSPARC-II®           | UltraSPARC-III®        |
|--------------------------|--------------------------|--------------------------|------------------------|
| <b>Year</b>              | 1995                     | 1997                     | 2000                   |
| <b>Architecture</b>      | SPARC V9, 4-issue        | SPARC V9, 4-issue        | SPARC V9, 4-issue      |
| <b>Die size</b>          | 17.7x17.8mm <sup>2</sup> | 12.5x12.5mm <sup>2</sup> | 15x15.5mm <sup>2</sup> |
| <b># of transistors</b>  | 5.2M                     | 5.4M                     | 23M                    |
| <b>Clock Frequency</b>   | 167MHz                   | 330MHz                   | 1GHz                   |
| <b>Supply voltage</b>    | 3.3V                     | 2.5V                     | 1.6V                   |
| <b>Process</b>           | 0.5µm CMOS               | 0.35µm CMOS              | 0.15µm CMOS            |
| <b>Metal layers</b>      | 4 (Al)                   | 5 (Al)                   | 7 (Al)                 |
| <b>Power consumption</b> | <30W                     | <30W                     | <80W                   |

## UltraSPARC-III: Clocking


- Performance-driven high-power clock distribution
- Eight logic gates per cycle
- High-speed semi-dynamic flip-flops with logic embedding
- Large hold time mandates use of advanced tools for fixing fast-path violations

## UltraSPARC-III®: Clocking

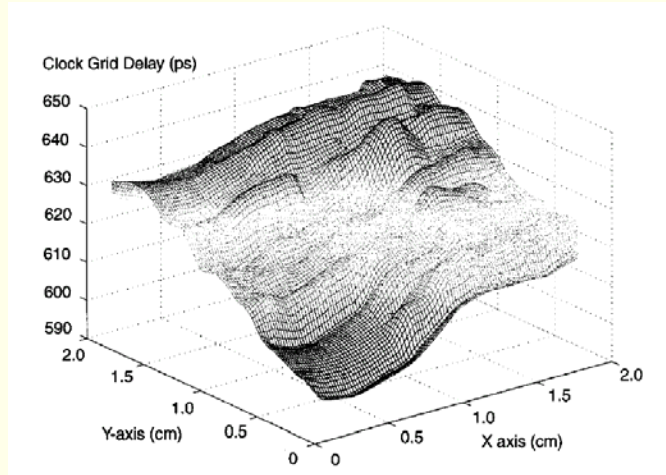

*Clock distribution delay in UltraSPARC-III (Heald et al. 2000), Copyright © 2000 IEEE*

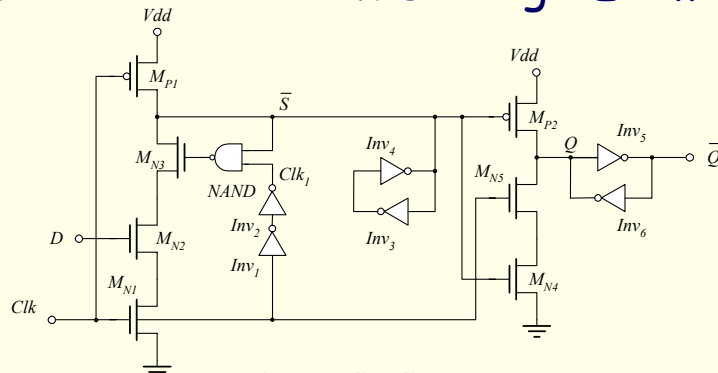
## UltraSPARC-III: Clock Storage Elements




*Semidynamic flip-flop (Klass 1998), Copyright © 1998 IEEE*

- Single-ended dynamic structure with use of keepers for static operation and use of clock pulsing
- Positive feedback (NAND) improves low-to-high setup time
- Fast, at the price of high internal and clock power

# UltraSPARC-III: Clock Storage Elements

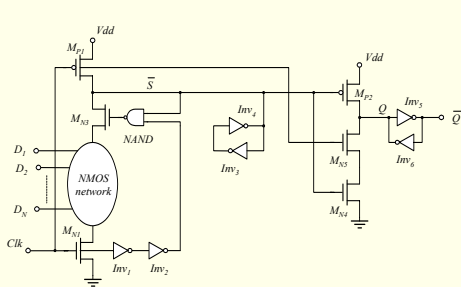

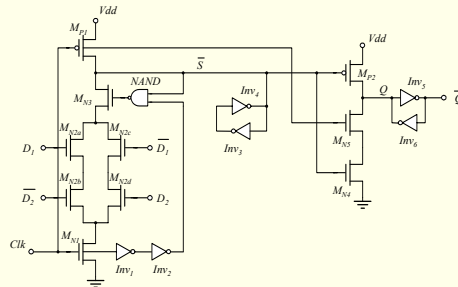Logic embedding in a semi-dynamic flip-flop




Two-input XOR function


(Klass, 1998), Copyright © 1998 IEEE

- A non-inverting logic function can be embedded by replacing the input D transistor with an n-MOS logic network
- Necessary for fitting 8 logic stages in cycle time, also used for scan
- Complexity of embedded logic limited by the n-MOS stack depth

# UltraSPARC-III: Clock Storage Elements

 

Single-ended dynamic SDFF

 


Differential dynamic SDFF

(Klass, 1998), Copyright © 1998 IEEE

- Dynamic version of SDFF used in dynamic logic paths
- Outputs exercise precharge-evaluate sequence to ensure monotonicity
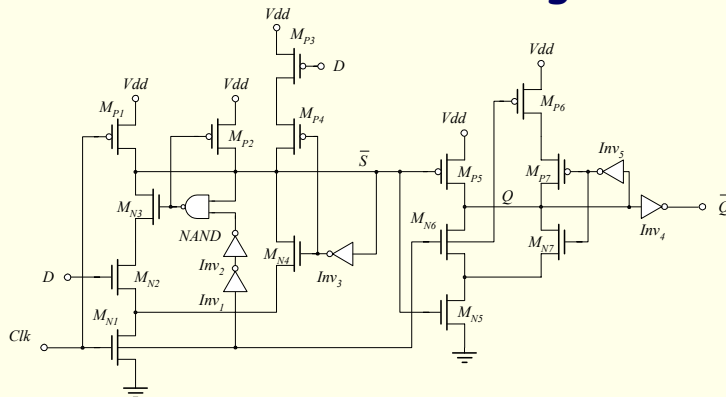
## UltraSPARC-III: Clock Storage Elements



*UltraSPARC-III flip-flop  
(Heald et al. 2000), Copyright © 2000 IEEE*

- Final UltraSPARC-III flip-flop modified by decoupling keepers to increase immunity to  $\alpha$ -particles
- Somewhat degraded speed and logic embedding property


## Microprocessor Examples

- Clocking for Intel® Microprocessors
  - IA-32 Pentium® Pro
  - First IA-64 Microprocessor
  - Pentium 4
- Sun Microsystems UltraSPARC-III® Clocking
  - Clocking and CSEs
- Alpha® Clocking: A Historical Overview
  - Clocking and CSEs
- IBM® Microprocessors
  - Level-Sensitive Scan Design
  - Examples of CSEs


# Alpha® Microprocessor Features

|                             | 21064     | 21164     | 21264     | 21364     |
|-----------------------------|-----------|-----------|-----------|-----------|
| # transistors [M]           | 1.68      | 9.3       | 15.2      | 152       |
| Die Size [mm <sup>2</sup> ] | 16.8x13.9 | 18.1x16.5 | 16.7x18.8 | 21.1x18.8 |
| Process                     | 0.75μm    | 0.5μm     | 0.35μm    | 0.18μm    |
| Supply [V]                  | 3.3       | 3.3       | 2.2       | 1.5       |
| Power [W]                   | 30        | 50        | 72        | 125       |
| Clk Freq. [MHz]             | 200       | 300       | 600       | 1200      |
| Gates/Cycle                 | 16        | 14        | 12        | 12        |


# Alpha® Microprocessors: Clocking

 

(a)

 


(b)

 

(c)


*Alpha microprocessor final clock driver location:  
(a) 21064, (b) 21164, (c) 21264*

# Alpha® Microprocessors: Clocking

 

*21064 clock skew*  
(Gronowski et al. 1998), Copyright © 1998 IEEE


# Alpha® Microprocessors: Clocking

 

*21164 clock skew*  
(Gronowski et al. 1998), Copyright © 1998 IEEE




# Alpha® Microprocessors: Clocking

 


21264 clock hierarchy  
(Gronowski et al. 1998), Copyright © 1998 IEEE

# Alpha® Microprocessors: Clocking

 


21264 clock skew  
(Gronowski et al. 1998), Copyright © 1998 IEEE

# Alpha® Microprocessors: Clocking

 


21364 major clock domains  
(Xanthopoulos et al. 2001), Copyright © 2001

# Alpha® Microprocessors: Clocking

 


21364, NCLK clock skew  
(Xanthopoulos et al. 2001), Copyright © 2001 IEEE

# Alpha® $\mu$ P: Clock Storage Elements

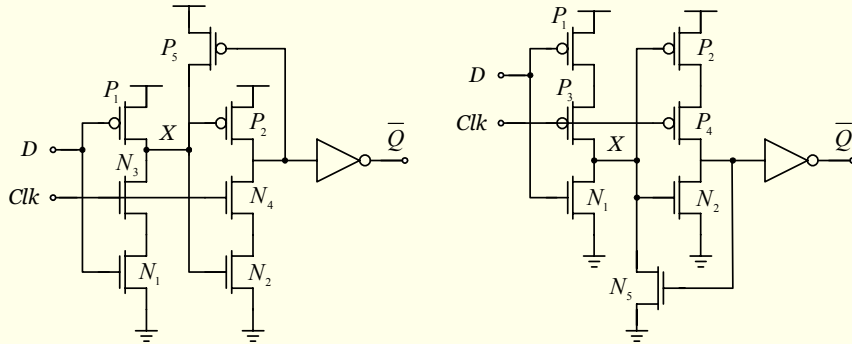

21064 modified TSPC latches  
(Gronowski et al. 1998), Copyright © 1998

# Alpha® $\mu$ P: Clock Storage Elements

 


(a)

(b)


21164: (a) phase-A latch, (b) phase-B latch  
(Gronowski et al. 1998), Copyright © 1998 IEEE
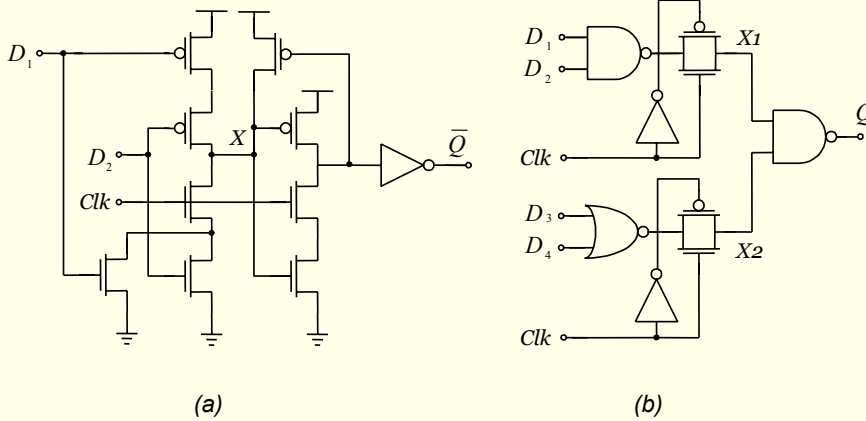
## Alpha® $\mu$ P: Clock Storage Elements




*Embedding of logic into a latch:  
 (a) 21064 TSPC latch, one level of logic;  
 (b) 21164 latch, two levels of logic.  
 (Gronowski et al. 1998), Copyright © 1998 IEEE*
 
## Alpha® $\mu$ P: Clock Storage Elements



*21264 flip-flop  
 (Gronowski et al. 1998), Copyright © 1998 IEEE*

# Alpha® Microprocessors: Timing

 

### Critical Path Definition and Criteria

- Identify common clock, D and R
- Maximize D
- Minimize R

$$D + U - R \leq T_{\text{cycle}}$$

### Race Definition and Criteria

- Identify common clock, D and R
- Minimize D
- Maximize R


$$D \geq R + H$$

*Critical-path and race analysis for clock buffering and conditioning  
(Gronowski et al. 1998), Copyright © 1998 IEEE*

# Microprocessor Examples


- Clocking for Intel® Microprocessors
  - IA-32 Pentium® Pro
  - First IA-64 Microprocessor
  - Pentium 4
- Sun Microsystems UltraSPARC-III® Clocking
  - Clocking and CSEs
- Alpha® Clocking: A Historical Overview
  - Clocking and CSEs
- IBM® Microprocessors
  - Level-Sensitive Scan Design
  - Examples of CSEs

## Hazard-Free Level-Sensitive Polarity-Hold Latch

 


*Eichelberger 1983*


## General LSSD Configuration

 


# LSSD Shift Register Latch

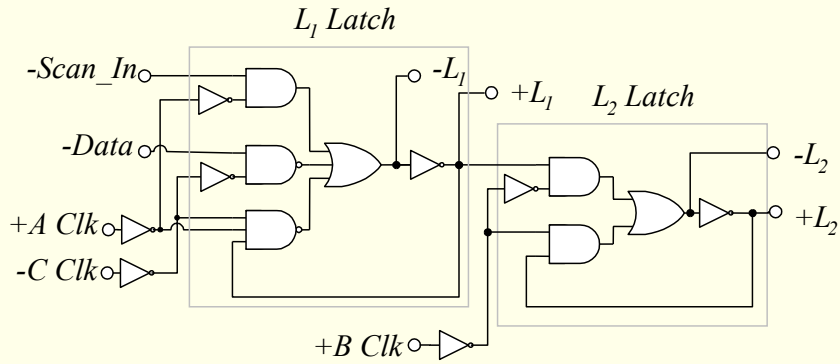

# LSSD Double Latch Design

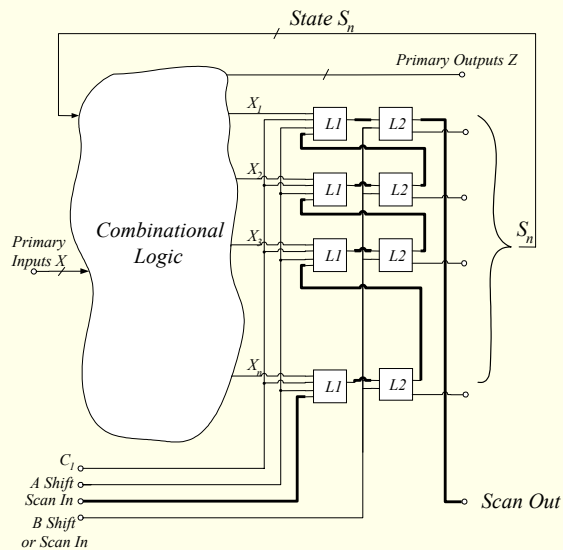


# IBM® S/390 Parallel Server Processor

 

*LSSD SRL with multiplexer used in the IBM S/390 G4 processor (Sigal et al. 1997), reproduced by permission*


# IBM® S/390 Parallel Server Processor

 

*Static multiplexer version of the SRL used in the IBM S/390 G4 (Sigal et al. 1997), reproduced by permission*




# IBM® S/390 Parallel Server Processor

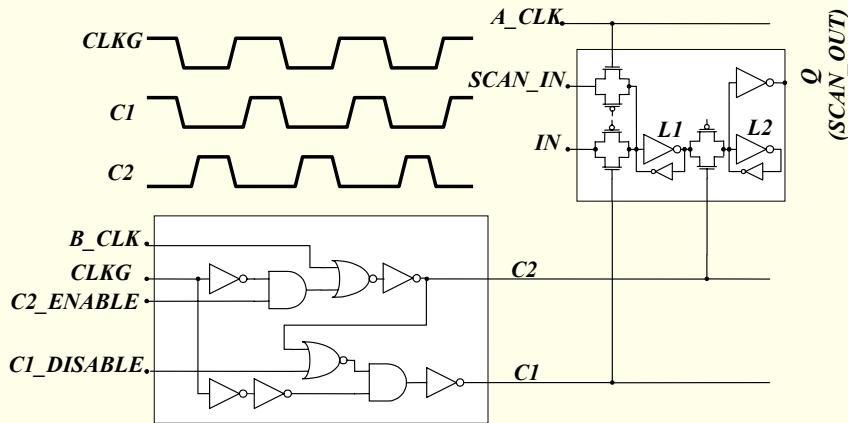


*A clocked storage element is used in the non-timing-critical timing macros of the IBM S/390 G4 processor (Sigal et al. 1997), reproduced by permission*

# IBM® S/390 Parallel Server Processor

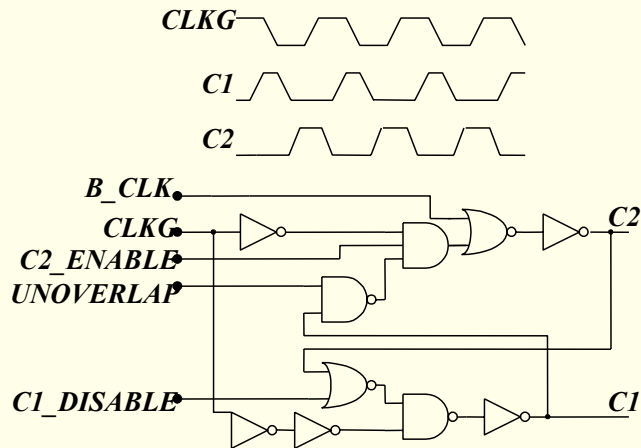


*The clock-generation element used to detect problems created with fast paths: IBM S/390 G4 processor (Sigal et al. 1997), reproduced by permission*

# IBM® PowerPC Processor

 


*The experimental IBM PowerPC processor  
(Silberman et al. 1998), reproduced by permission*

# IBM® PowerPC 603: Master-Slave Latch

 

*The PowerPC 603 MSL  
(Gerosa et al. 1994), Copyright © 1994 IEEE*

## IBM® PowerPC 603: Local Clk Generator

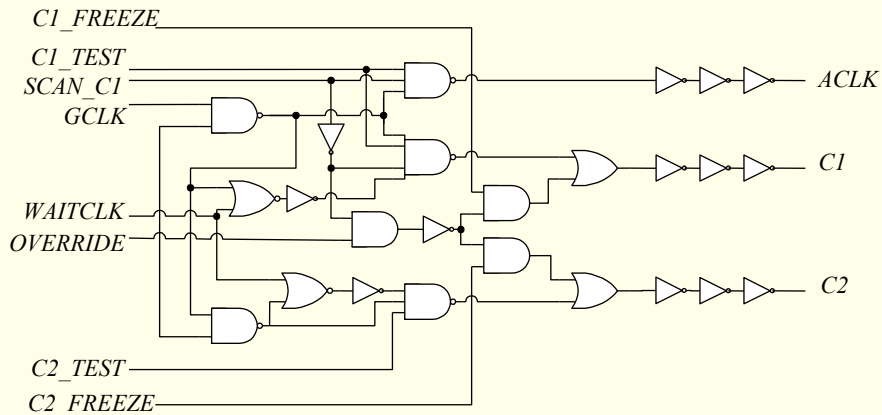

*The PowerPC 603 local clock regenerator  
(Gerosa et al. 1994), Copyright © 1994 IEEE*

## Summary

- Intel® Microprocessors
  - Active clock deskewing in Pentium® processors
- Sun Microsystems® Processors
  - Semidynamic flip-flop (one of the fastest single-ended flip-flops today, "soft-edge")
- Alpha® Processors
  - Performance leader in the '90s
  - Incorporating logic into CSEs
- IBM® Processors
  - Design for testability techniques
  - Low-power champion PowerPC 603